

本製品は、ルネサス エレクトロニクス製のプログラミング機能付きオンチップ・デバッグ・エミュレータ E1 を使用して、マイコンの動作を試すためのターゲット・ボードです。


①RL78/G1E ターゲット・ボード(QB-R5F10FME-TB)の特徴

- RL78/G1E(R5F10FMED)搭載
- メイン・クロック 20MHz(発振子を利用)で動作可能(2.7V~5.5V 供給時)
- ユニバーサル・エリア(2.54mm ピッチ)を搭載
- フラッシュ・メモリ・プログラミング、オンチップ・デバッグに両対応(TOOL0 端子使用)
- マイコンの端子を周辺ボード・コネクタに配置した高拡張性
- 鉛(Pb)フリー対応品

②ハードウェア仕様

CPU R5F10FMEAFB	メイン・クロック動作周波数	20MHz(ボード上の発振子を使う場合)
搭載部品	CN1,CN2: 周辺ボードコネクタ(2.54mm ピッチ) 50pin ソケット x2(パッドのみ)	
	CN3: 14pin コネクタ(E1 接続用)	
	Power LED: 赤 x1(LED3)	
	評価用 LED: 黄 x2(LED1 は P41,LED2 は P42 へ接続)	
	評価用 SW: SW1(INTP0 へ接続)	
	メイン・クロック(OSC1): 20MHz 発振子(X1,X2 へ接続)	
動作電圧	2.7V~5.5V(OSC1:20MHz 発振子使用時)	

③寸法、部品配置など

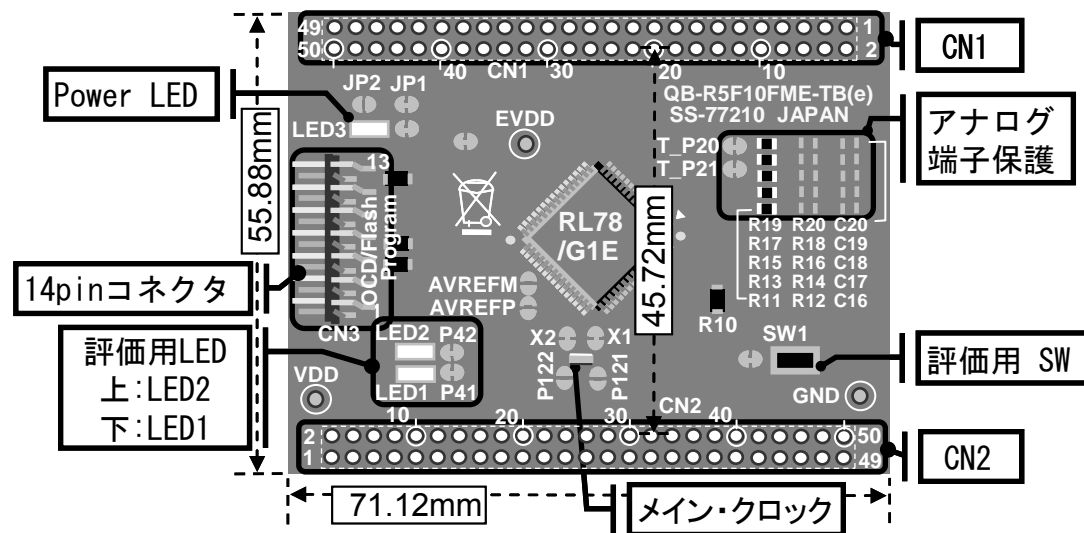

基板上のパターン について:パターンをカットすることで、その回路はオープンとなります。

再度接続させたい場合は半田ショートしてください。

P41,P42 を使用する場合は LED の右のショートパッドをパターンカットしてください。

④使用上の注意

- ・VDD と AVDD をショートパッドで分離可能ですが、分離した場合でも VDD と AVDD は同電位で使用してください。
- ・本製品に関するサポートはお受けしておりません。初期不良の場合に限り、交換いたします。

The QB-R5F10ELE-TB is a target board used for evaluating microcontroller operations, using the E1, the Renesas Electronics on-chip debug emulator with programming function (hereinafter referred to as E1).


(1) RL78/G1E target board (QB-R5F10FME-TB) features

- Incorporates RL78/G1E (R5F10FMED).
- A 20 MHz resonator mounted as main clock, high-speed operation enabled (@ 2.7 to 5.5 V)
- Equipped with universal area (2.54 mm pitch)
- Supports both flash memory programming and on-chip debugging (using TOOL0 pin)
- Highly extendable; peripheral board connectors are equipped with microcontroller pins
- Lead-free (Pb-free) product

(2) hardware specifications

CPU R5F10FMEAFB	Main clock operating frequency	20 MHz. (when use resonator mounted on board)
Embedded parts	CN1, CN2: Peripheral board connectors (2.54 mm pitch), 50-pin socket x 2 (pad only)	
	CN3: 14-pin connector (for E1 connection)	
	Power LED: Red x 1 (LED3)	
	Test LED: Yellow x 2 (LED1 connected to P41, LED2 connected to P42)	
	Test SW: SW1 (connected to INTP0)	
	Main clock (OSC1): 20 MHz resonator(connected to X1 and X2)	
Operating voltage	2.7 to 5.5 V(when 20MHz resonator used at OSC1)	

(3) Dimensions and parts layout

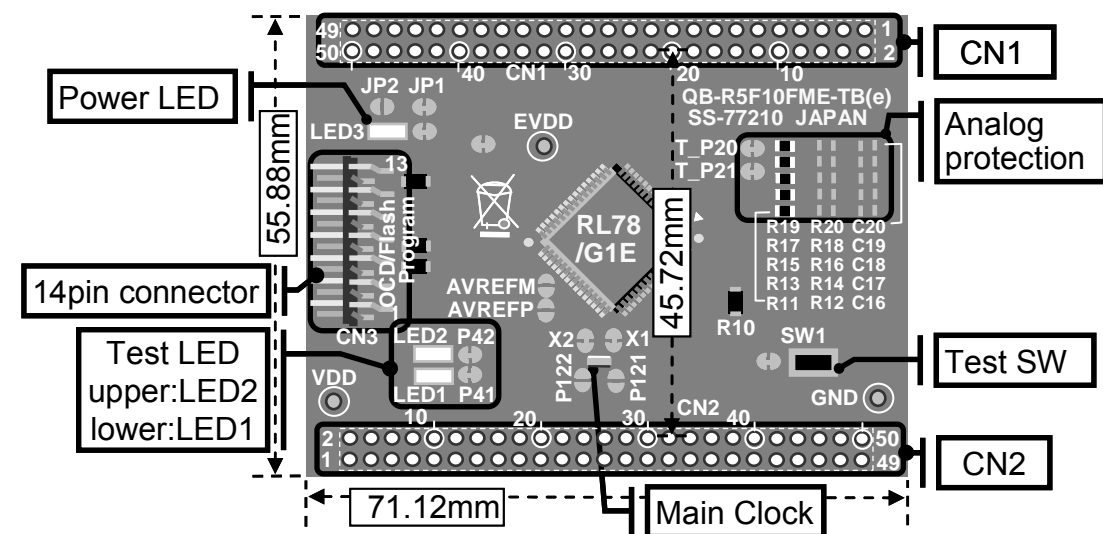

Pattern on the board: Splitting this wiring leaves open the relevant circuit.

To reconnect the circuit, short the circuit by soldering.

When using P41 and P42, cut off the short pad on the right side of LED.

(4) Notes on use

- VDD and AVDD can be divided by using short pad, but the voltage level of them must be same level if they are divided.
- Renesas Electronics will not provide any support for this board, but the board can be exchanged with a new product only when it has an initial failure.

